

Code No: R07A1EC05

**R07****Set No. 2**

I B.Tech Examinations, December 2010

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. Define average value and obtain the same for a half wave rectified voltage wave. [16]
2. Determine the Z parameters of the network shown in figure 2. [16]

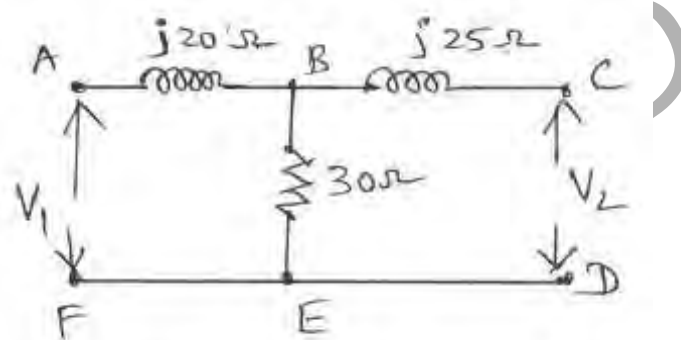


Figure 2

3. State and Explain with proof of Reciprocity Theorem. [16]
4. A prototype HPF has cut-off frequency 6 KHz and design impedance 300 Ohms. Calculate L & C? [16]
5. (a) Define half power frequency. Draw a sketch and explain.  
(b) Derive the formula for half power frequencies. [6+10]
6. For the figure 6 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]
7. For the network shown in figure 7, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

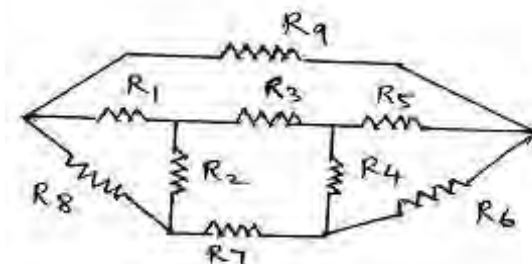


Figure 7

Code No: R07A1EC05

**R07**

**Set No. 2**

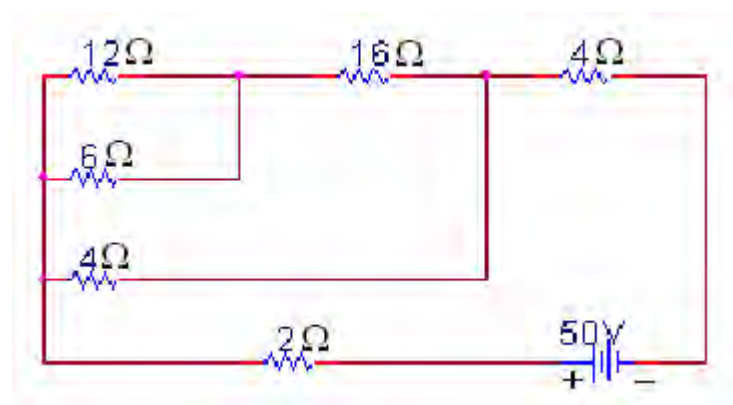


Figure 6:

8. Derive the step voltage response equation for a series RLC circuit. [16]

\*\*\*\*\*

JNTUWORLD

Code No: R07A1EC05

**R07****Set No. 4**

I B.Tech Examinations, December 2010

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. State and Explain with proof of Reciprocity Theorem. [16]
2. For the figure 2 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]

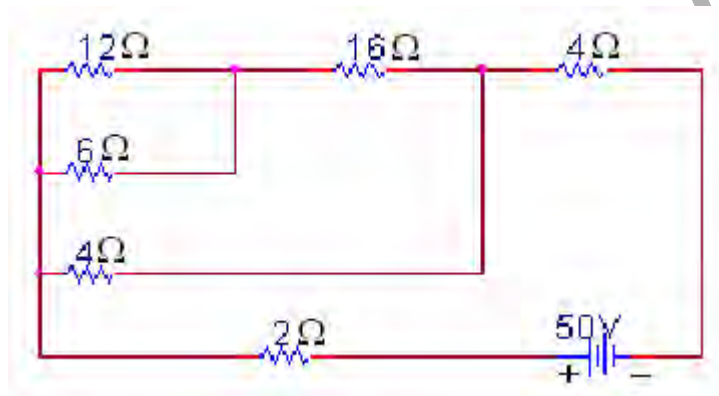


Figure 2:

3. (a) Define half power frequency. Draw a sketch and explain.  
(b) Derive the formula for half power frequencies. [6+10]
4. Define average value and obtain the same for a half wave rectified voltage wave. [16]
5. For the network shown in figure 5, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

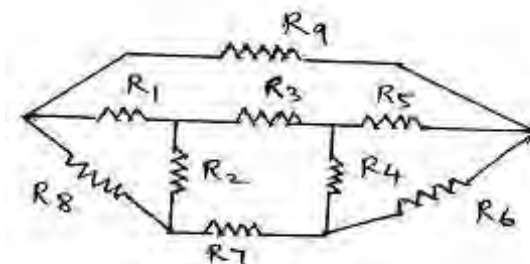


Figure 5

Code No: R07A1EC05

**R07****Set No. 4**

6. A prototype HPF has cut-off frequency 6 KHz and design impedance 300 Ohms. Calculate L & C? [16]
7. Determine the Z parameters of the network shown in figure 7. [16]

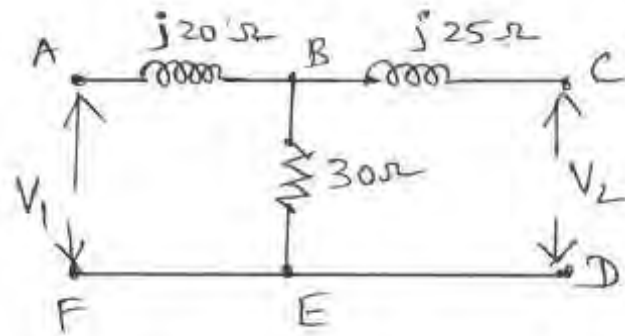


Figure 7

8. Derive the step voltage response equation for a series RLC circuit. [16]

\*\*\*\*\*

Code No: R07A1EC05

**R07****Set No. 1**

I B.Tech Examinations, December 2010

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. Define average value and obtain the same for a half wave rectified voltage wave. [16]
2. A prototype HPF has cut-off frequency 6 KHz and design impedance 300 Ohms. Calculate L & C? [16]
3. For the figure 3 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]

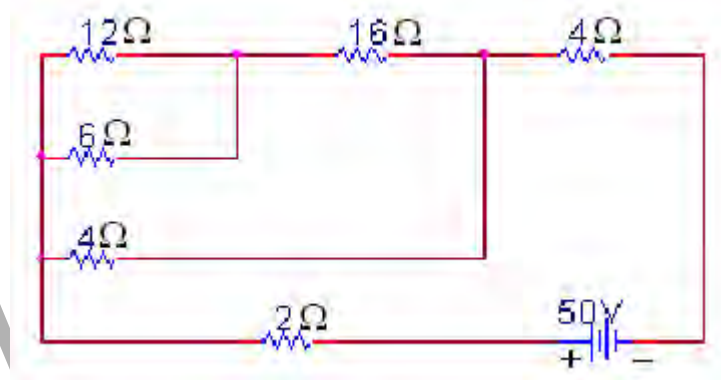


Figure 3:

4. Determine the Z parameters of the network shown in figure 4. [16]

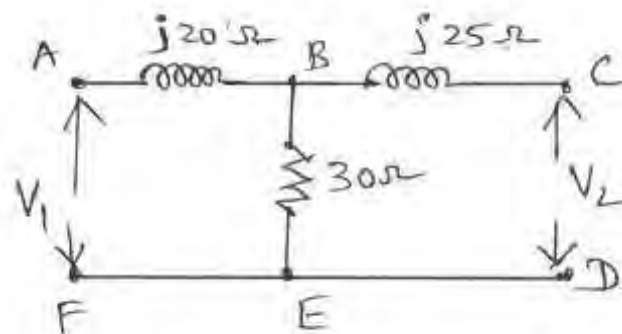


Figure 4

5. Derive the step voltage response equation for a series RLC circuit. [16]
6. (a) Define half power frequency. Draw a sketch and explain.

Code No: R07A1EC05

**R07****Set No. 1**

(b) Derive the formula for half power frequencies. [6+10]

7. For the network shown in figure 7, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

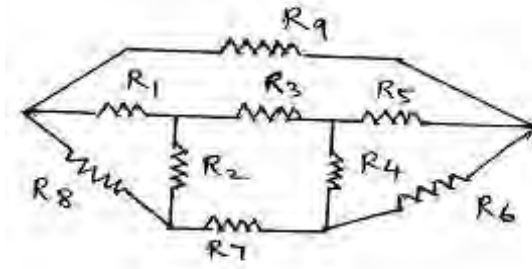


Figure 7

8. State and Explain with proof of Reciprocity Theorem. [16]

\*\*\*\*\*

Code No: R07A1EC05

**R07****Set No. 3**

I B.Tech Examinations, December 2010

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. Define average value and obtain the same for a half wave rectified voltage wave. [16]
2. State and Explain with proof of Reciprocity Theorem. [16]
3. For the figure 3 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]

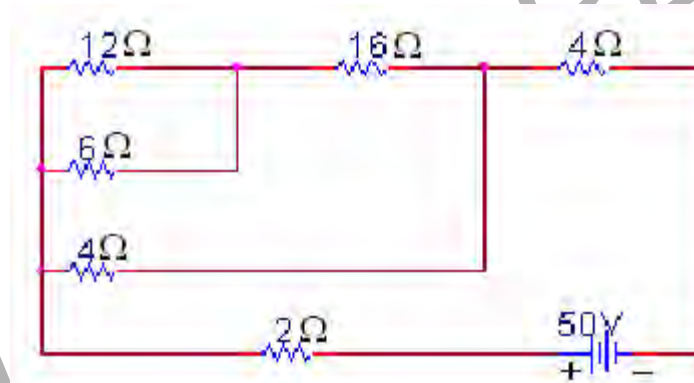


Figure 3:

4. A prototype HPF has cut-off frequency 6 KHz and design impedance 300 Ohms. Calculate L & C? [16]
5. For the network shown in figure 5, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

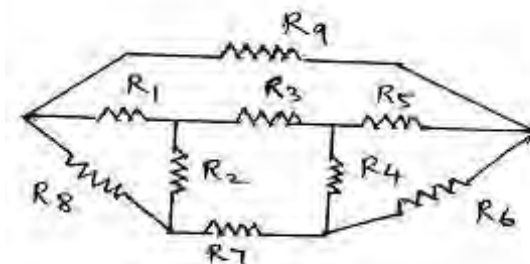


Figure 5

6. (a) Define half power frequency. Draw a sketch and explain.

Code No: R07A1EC05

**R07****Set No. 3**

- (b) Derive the formula for half power frequencies. [6+10]
7. Derive the step voltage response equation for a series RLC circuit. [16]
8. Determine the Z parameters of the network shown in figure 8. [16]

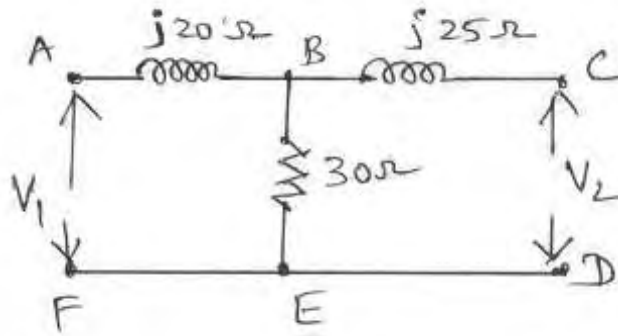


Figure 8

\*\*\*\*\*